
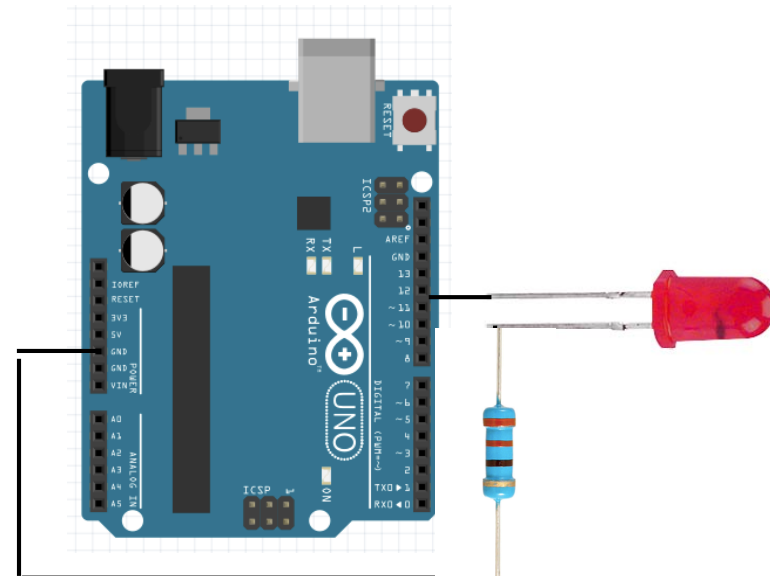
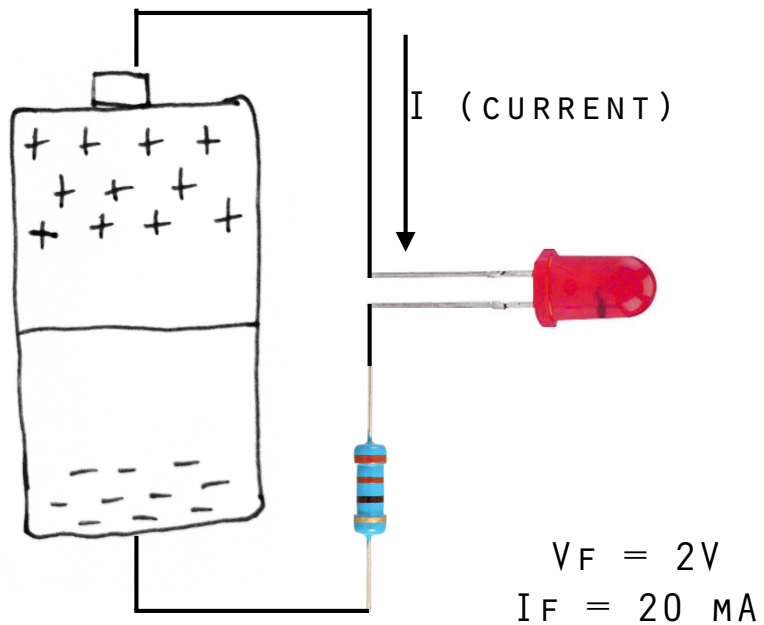
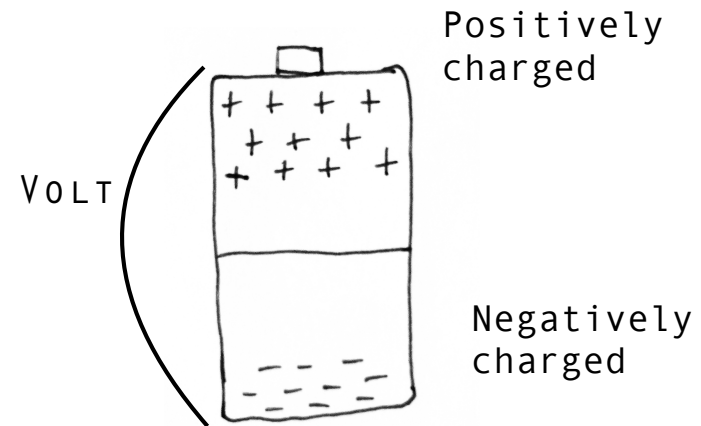


ELECTRONICS 1

ELECTRONICS FOR INTERACTIVE MEDIA DESIGN

EMMA PARESCHI


# POWER CONSUMPTION

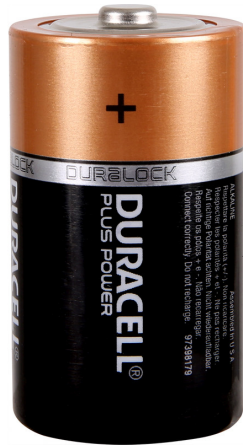
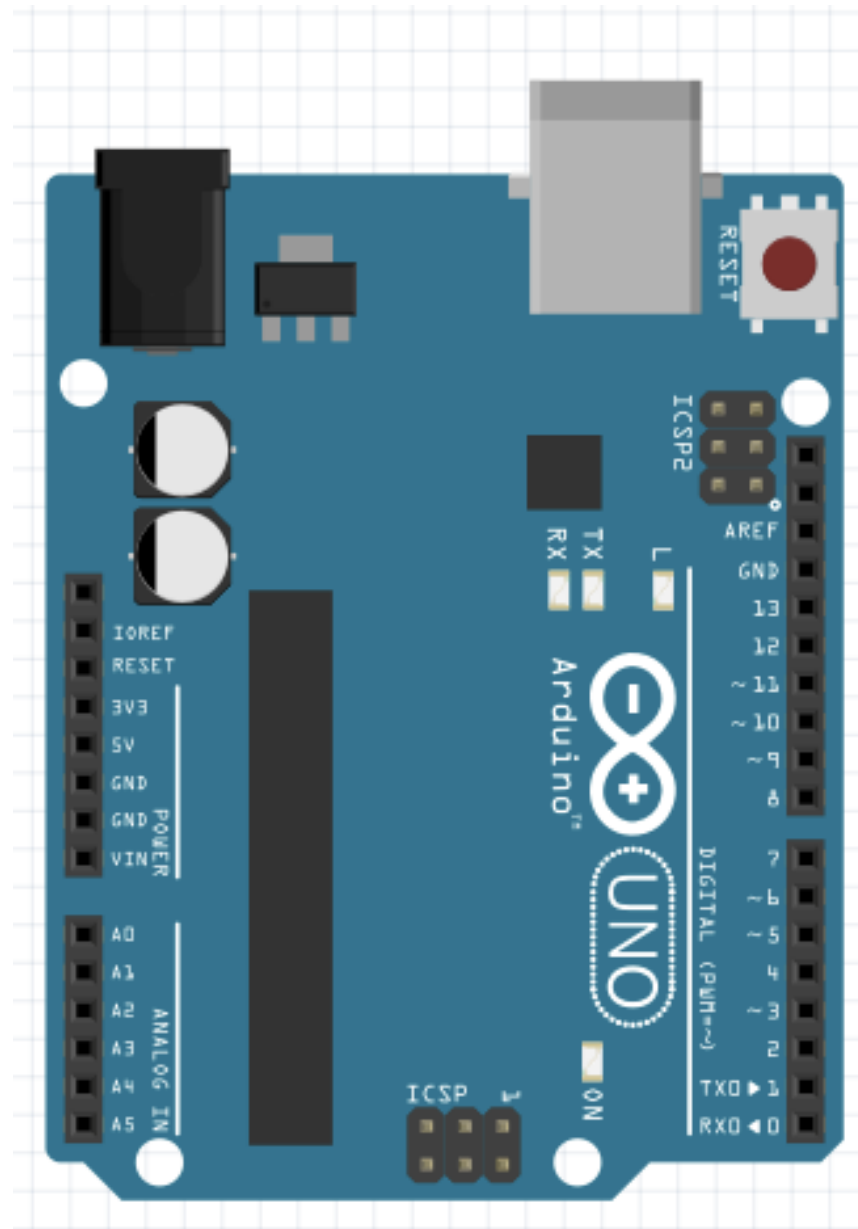
# POWER CAPABILITY OF ARDUINO UNO

Pin 5V:

- Powered by USB: max 500mA
- Powered by external battery or power supply: max 1A




I/O pins: max 40 mA

Sum of all input/output pins combined (but NOT including the "5V" pin): 200mA

# NODEMCU v2 - POWER PIN

I/O pins: max 12 mA

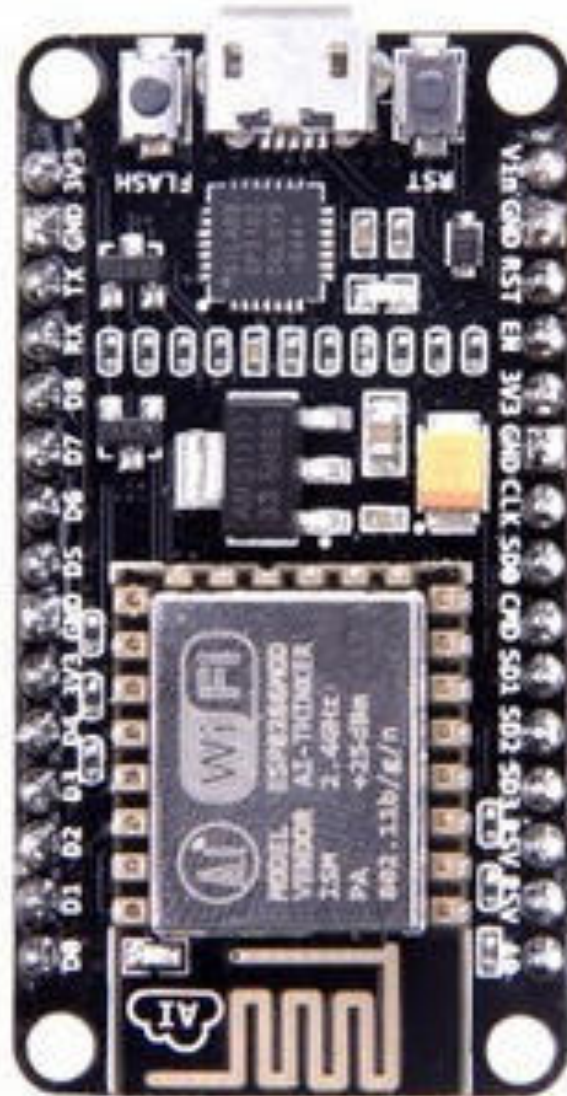

Pin Vin:

- Powered by USB: max 500mA

Pin 3V3:


- Powered by USB: max 500mA
- Powered by external battery or power supply: max 1A
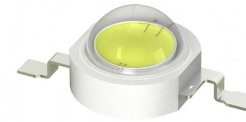
# LOW POWER / HIGH POWER



$V_F: 2V$   
 $I_F: \text{MAX } 20\text{mA}$

POWER:  $V_F * I_F$   
 $P = 0,04\text{W}$



$V_F: 3.2-3.4V$   
 $I_F: \text{MAX } 350\text{mA}$

POWER:  $V_F * I_F$   
 $P = 1,05\text{W}$

CAN YOU DRIVE IT WITH ARDUINO UNO?  
CAN YOU DRIVE IT WITH NODEMCU?

# POWER DEVICES: MOTORS

## SERVO MOTORS



9G




35Kg

## DC MOTORS



## STEPPER MOTORS

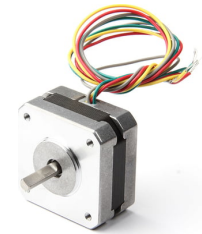


POWER SUPPLY: 3V-6V  
CURRENT > 500mA

# WHAT MAKES MOTORS MOVE?

MAGNETIC FIELD





MOTION

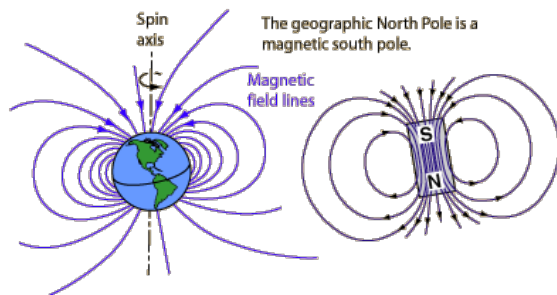

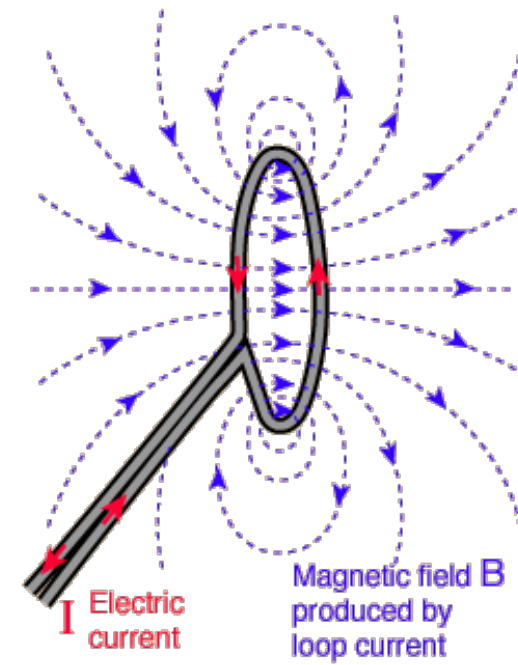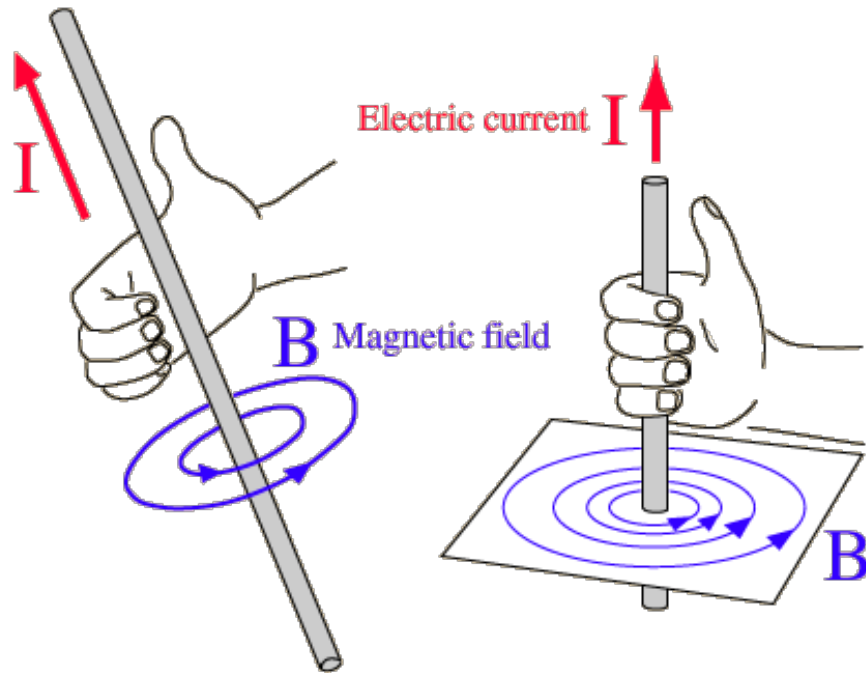
# ELECTROMAGNETISM

To create a magnet or magnetic field: current through a wire.









# ELECTROMAGNET

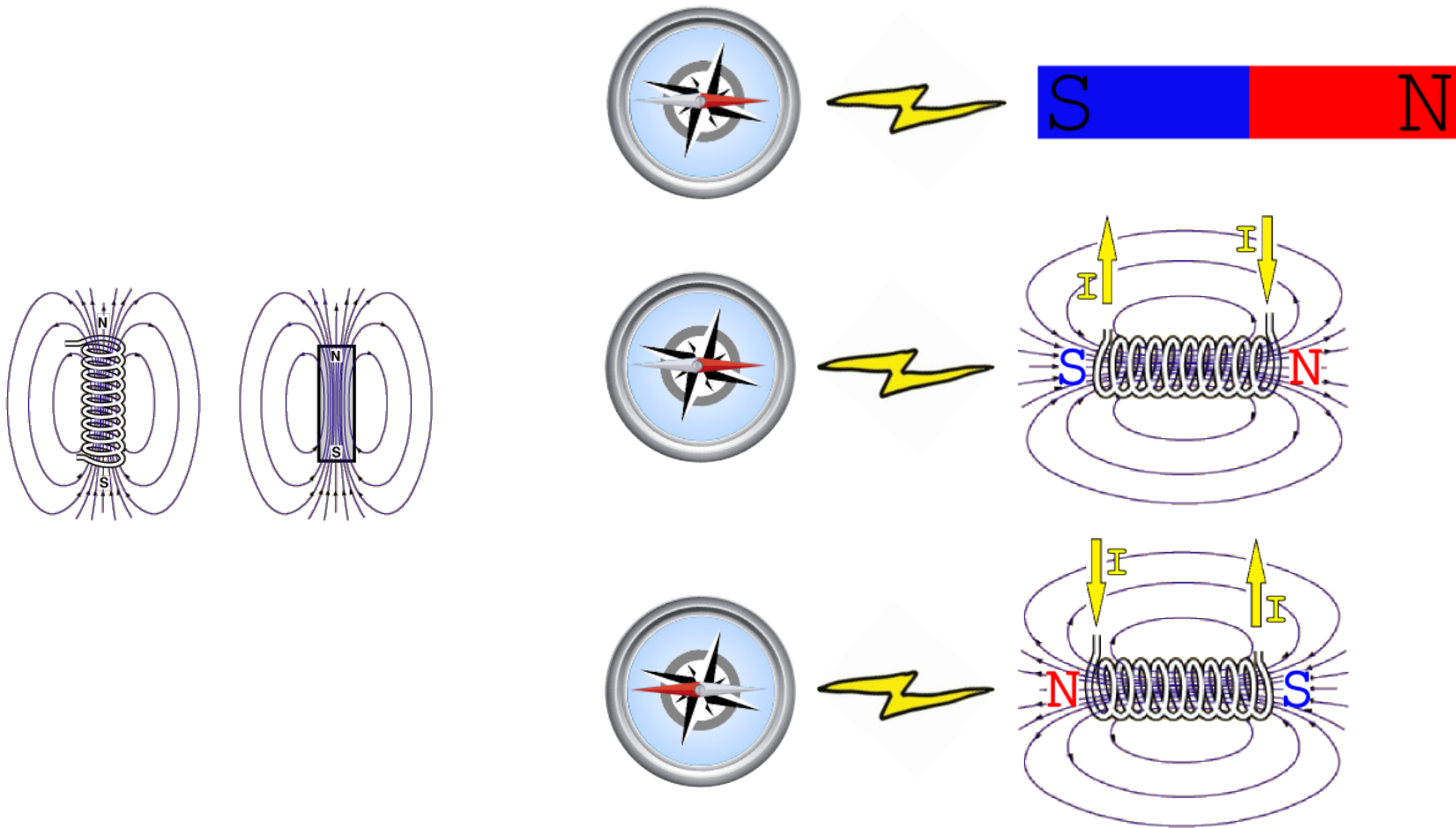



A SOLENOID WITH CURRENT = MAGNET!!!!

# ELECTROMAGNET

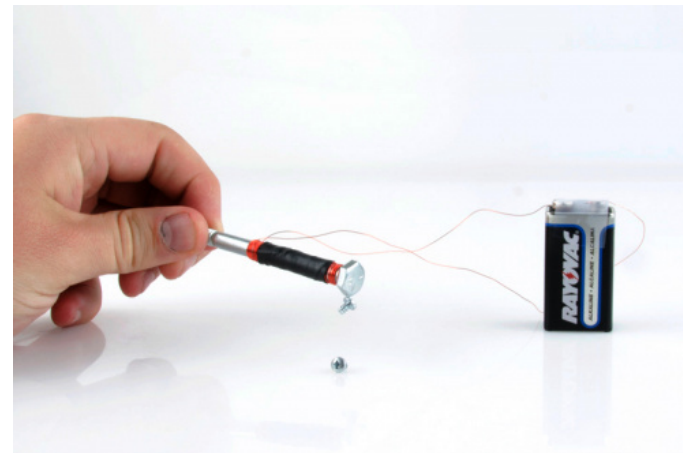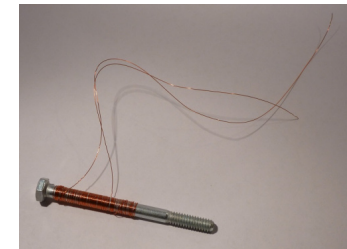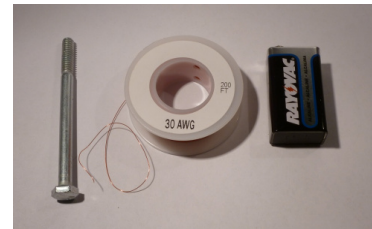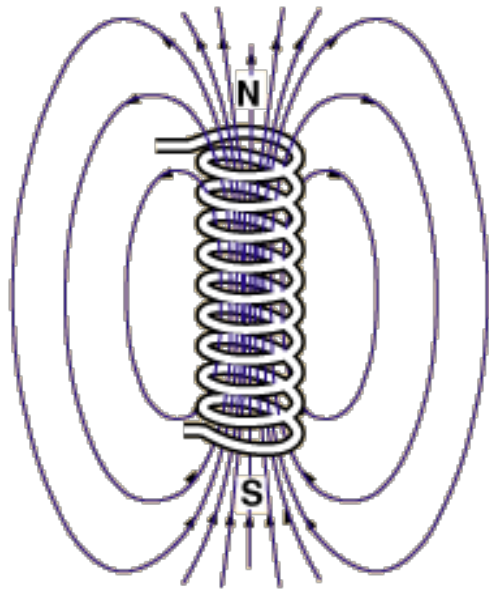

# DC BRUSHED MOTOR

CURRENT PER SOLENOIDS: 70mA

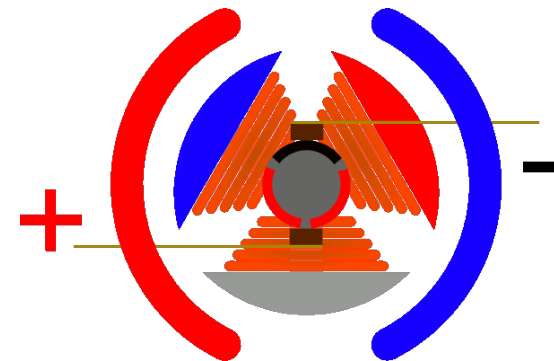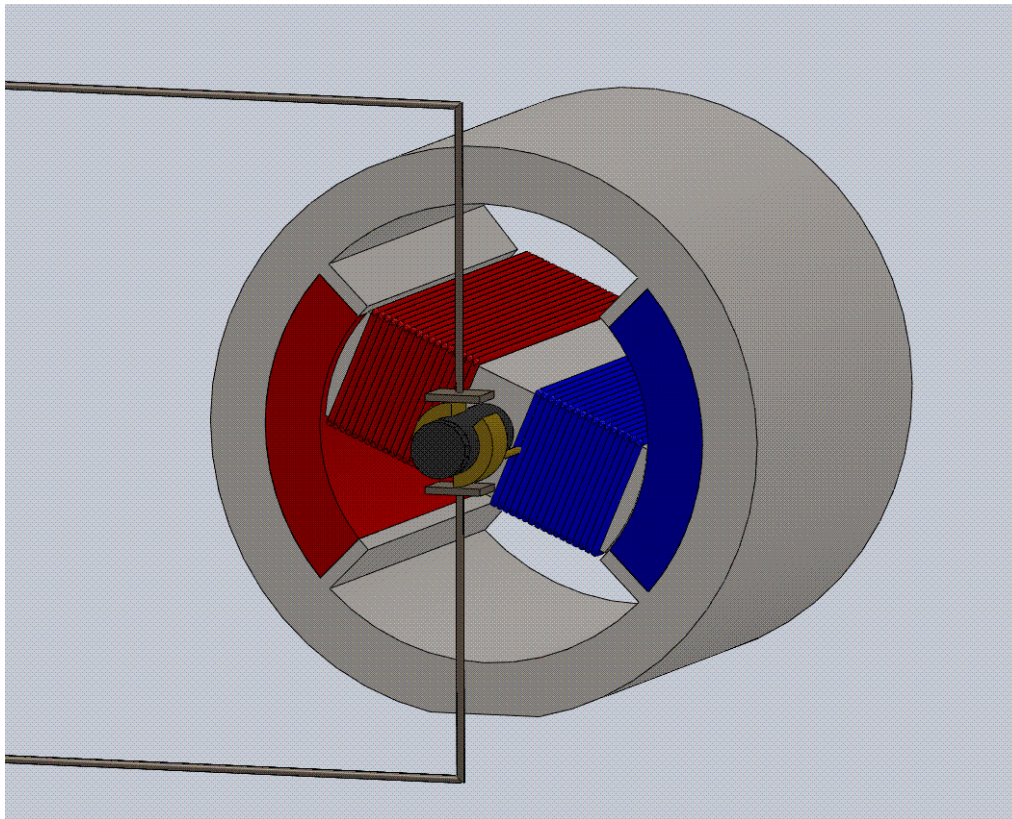

<https://nationalmaglab.org/education/magnet-academy/watch-play/interactive/dc-motor>

# HIGH POWER DRIVERS DEVICES: TRANSISTORS

THE TRANSISTORS ARE ACTIVE DEVICES AND THE BASIC BLOCKS OF ANY ELECTRONICS CIRCUIT.



—> AMPLIFIER

—> SWITCH CONTROLLED BY A VOLTAGE


BIPOLAR




TWO TYPES

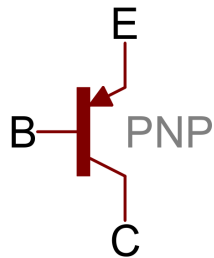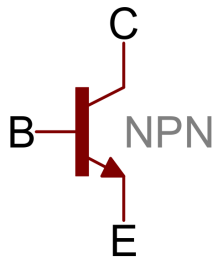


MOSFET

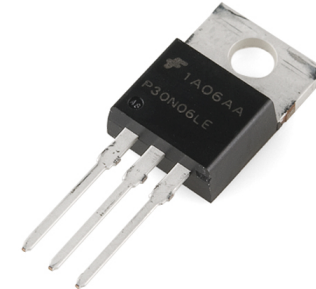

TWO TYPES


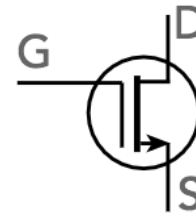


N - CHANNEL

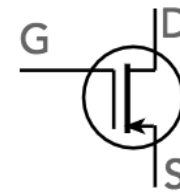


P - CHANNEL


# MOSFET N-CHANNEL

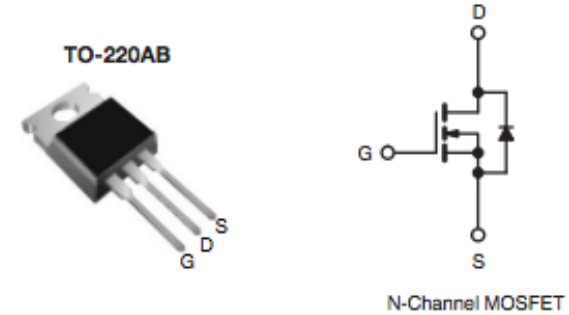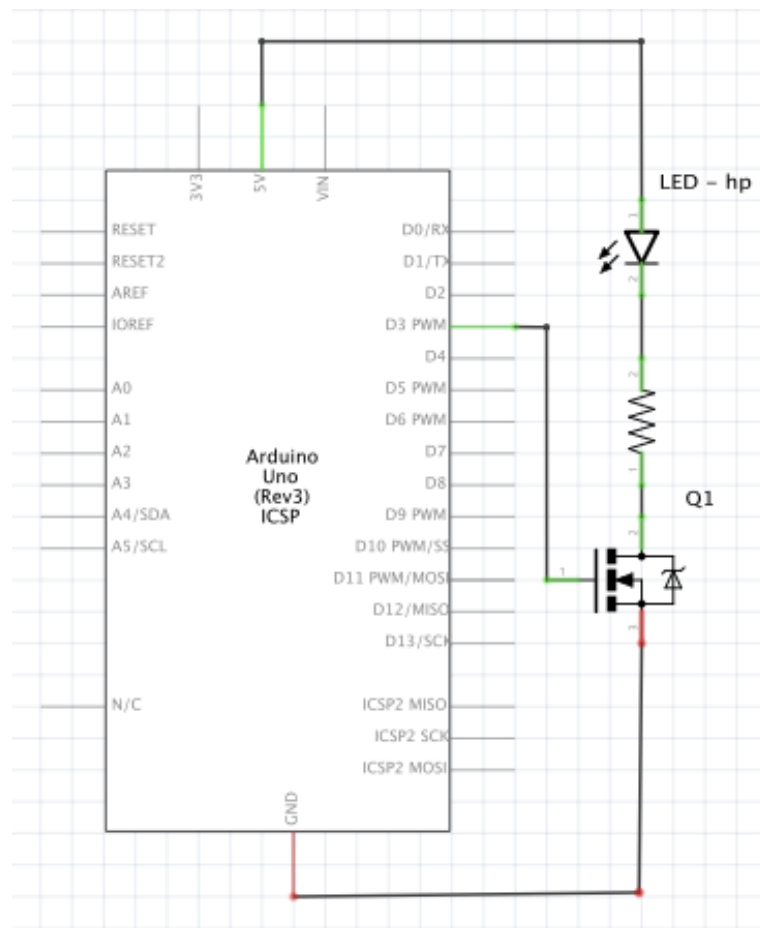


THREE TERMINALS:  
SOURCE  
GATE  
DRAIN

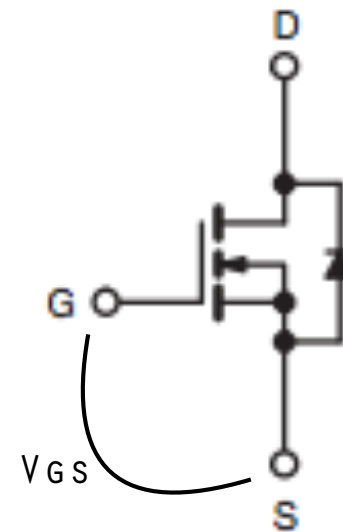

# MOSFET N-CHANNEL


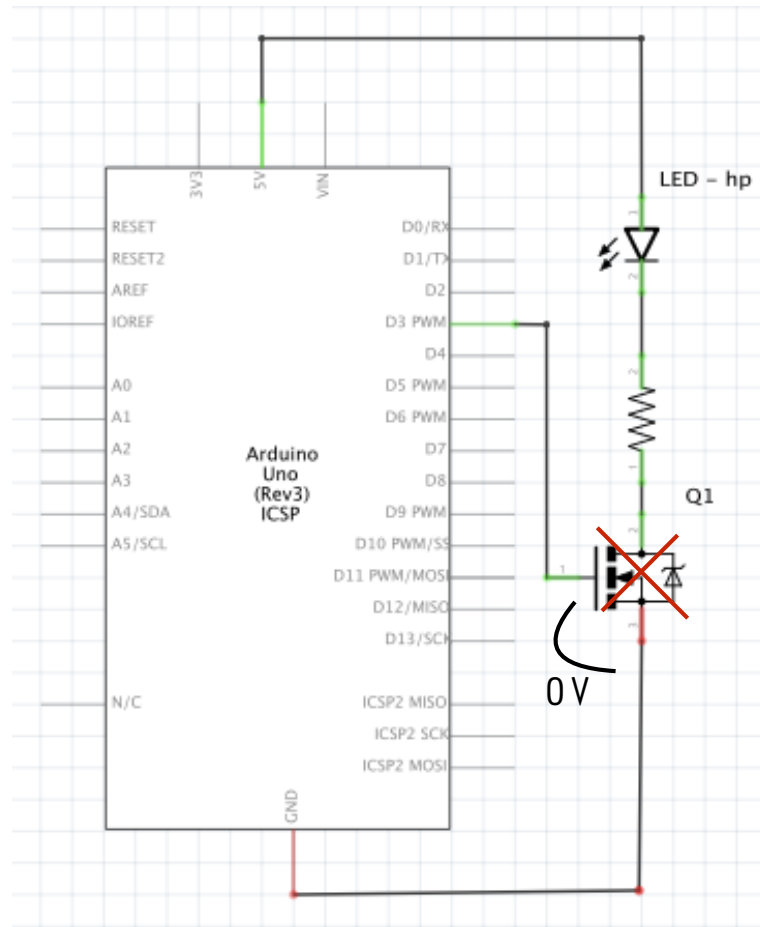


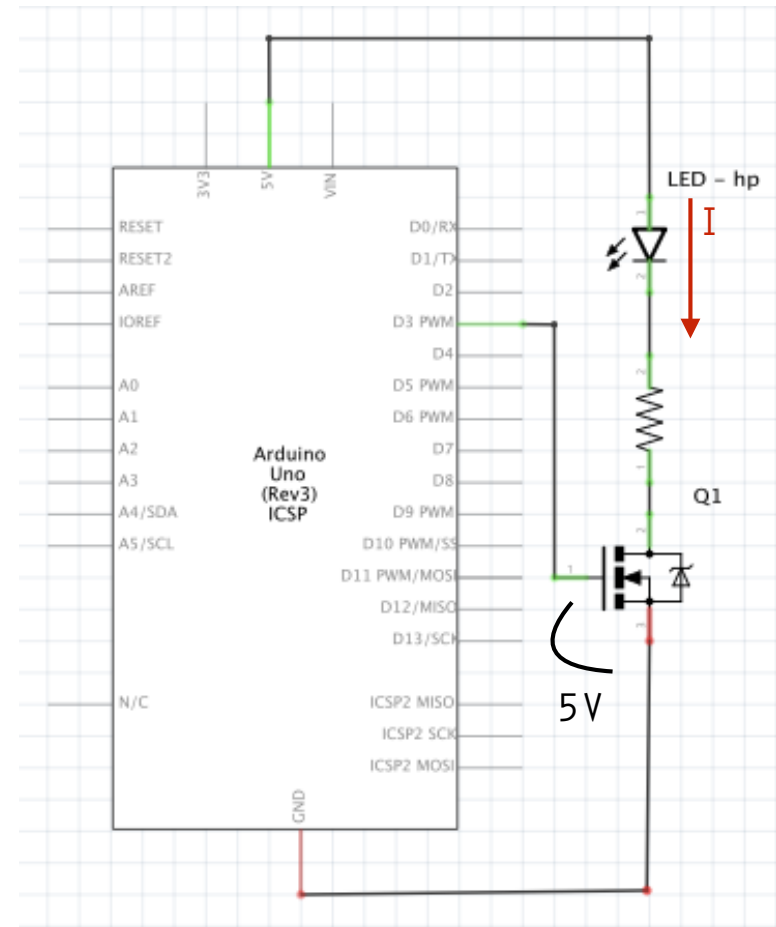IF  $V_{GS} = 0V$   
 $\Rightarrow$  OPEN LOOP, NO CURRENT





IF  $V_{GS} > 2V$   
 $\Rightarrow$  CLOSE LOOP, CURRENT

# DC MOTOR (BRUSHED) - SCHEMATIC - WRONG

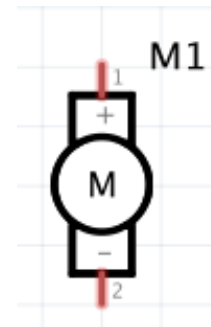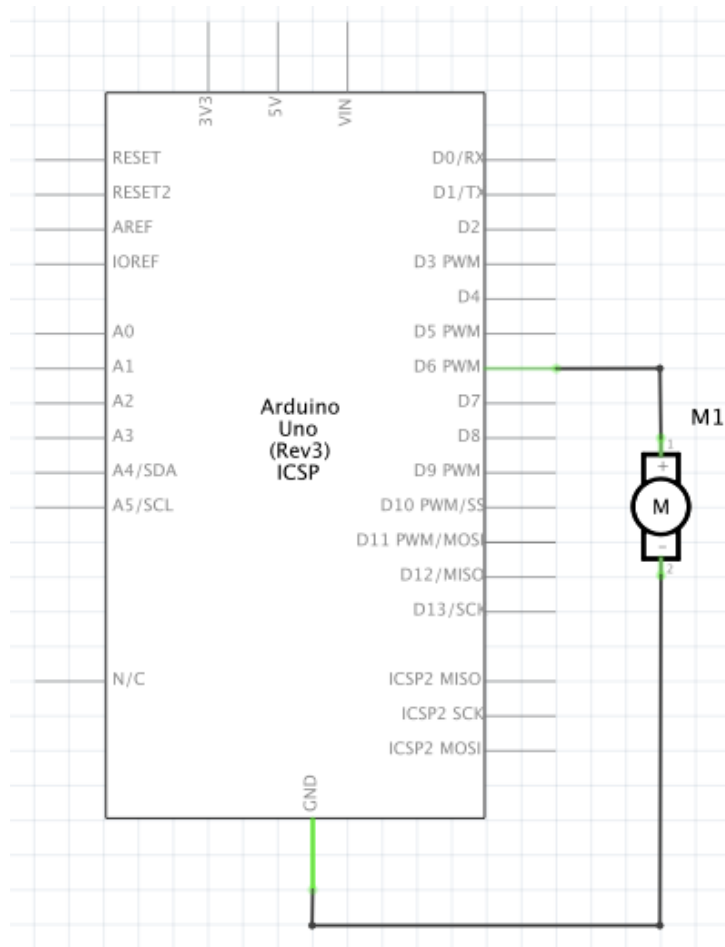


# DC MOTOR (BRUSHED) - SCHEMATIC - WRONG

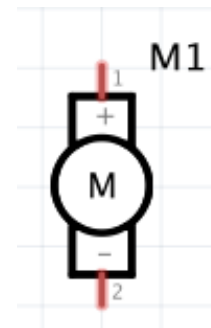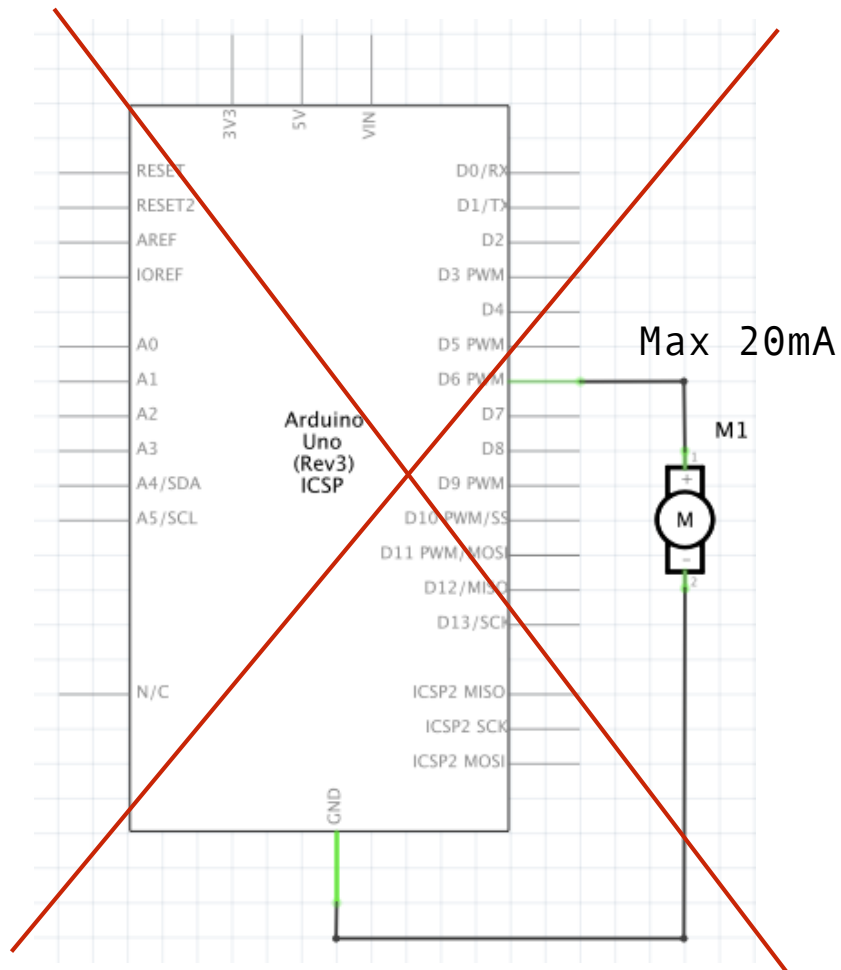



# DC MOTOR (BRUSHED) - SCHEMATIC

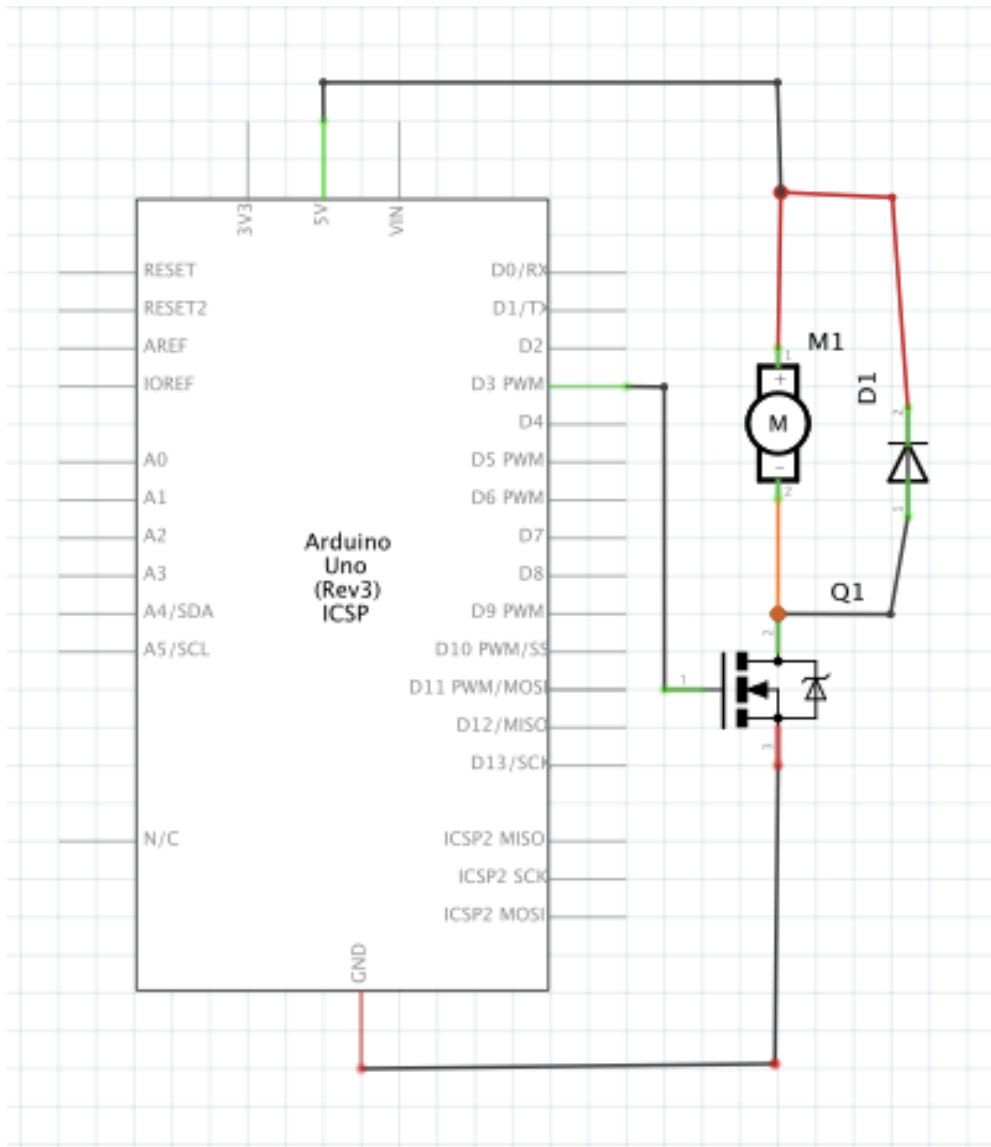

DIODE




# RELAY - 220V

A relay is an **electromagnetic** switch operated by a relatively small **electric** current that can turn on or off a much larger electric current. The heart of a relay is an electromagnet (a coil of wire that becomes a temporary **magnet** when electricity flows through it). You can think of a relay as a kind of electric **lever**: switch it on with a tiny current and it switches on ("leverages") another appliance using a much bigger current.



Mini SPDT Relay  
12V 10A 250V


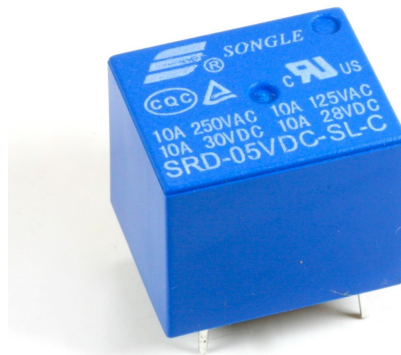


Mini SPDT Relay  
5V 10A 250V




Mini SPDT Relay  
24V 10A 250V


# RELAY - INSIDE

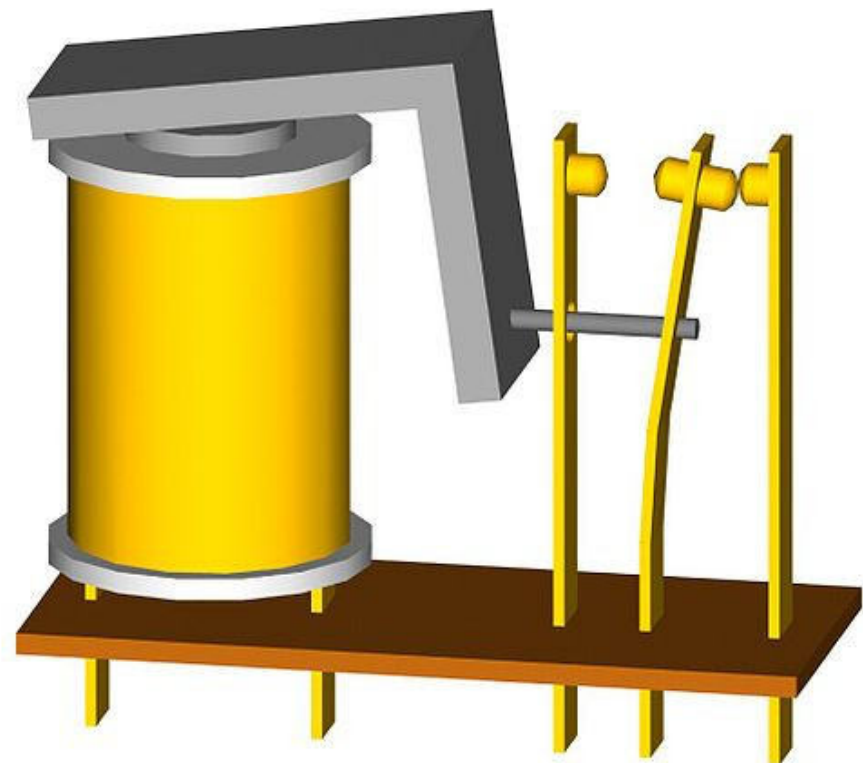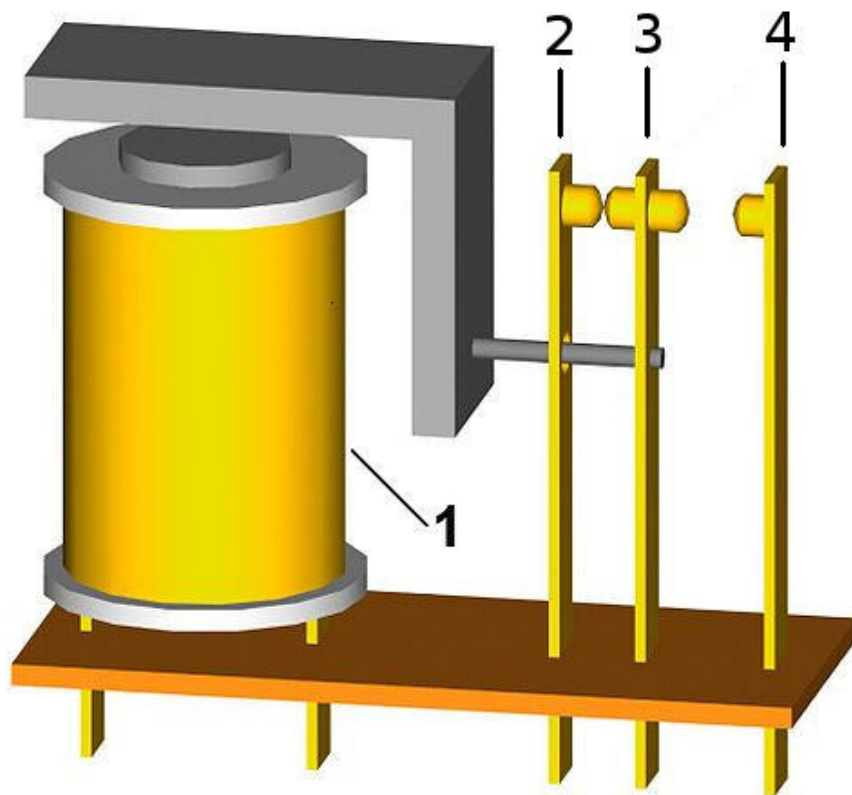


# RELAY - BREAKOUT BOARD

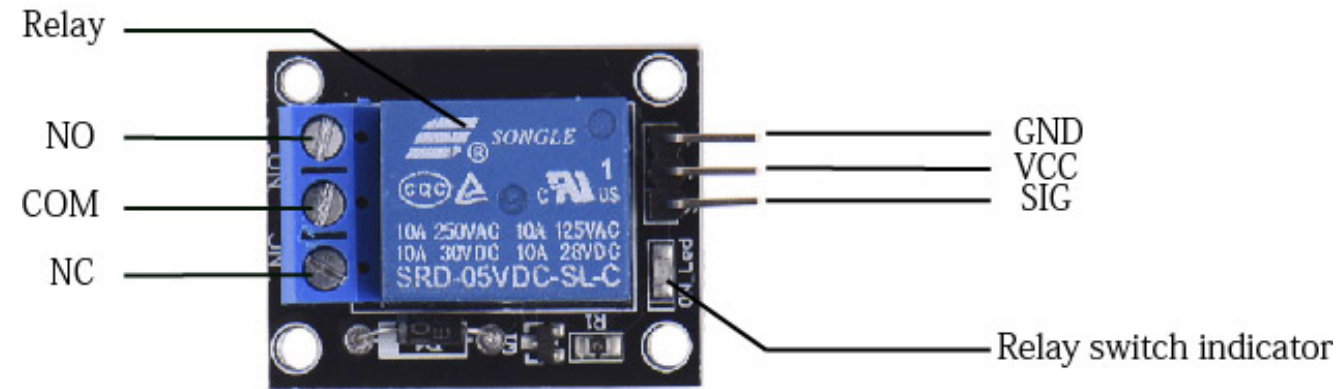

# RELAY

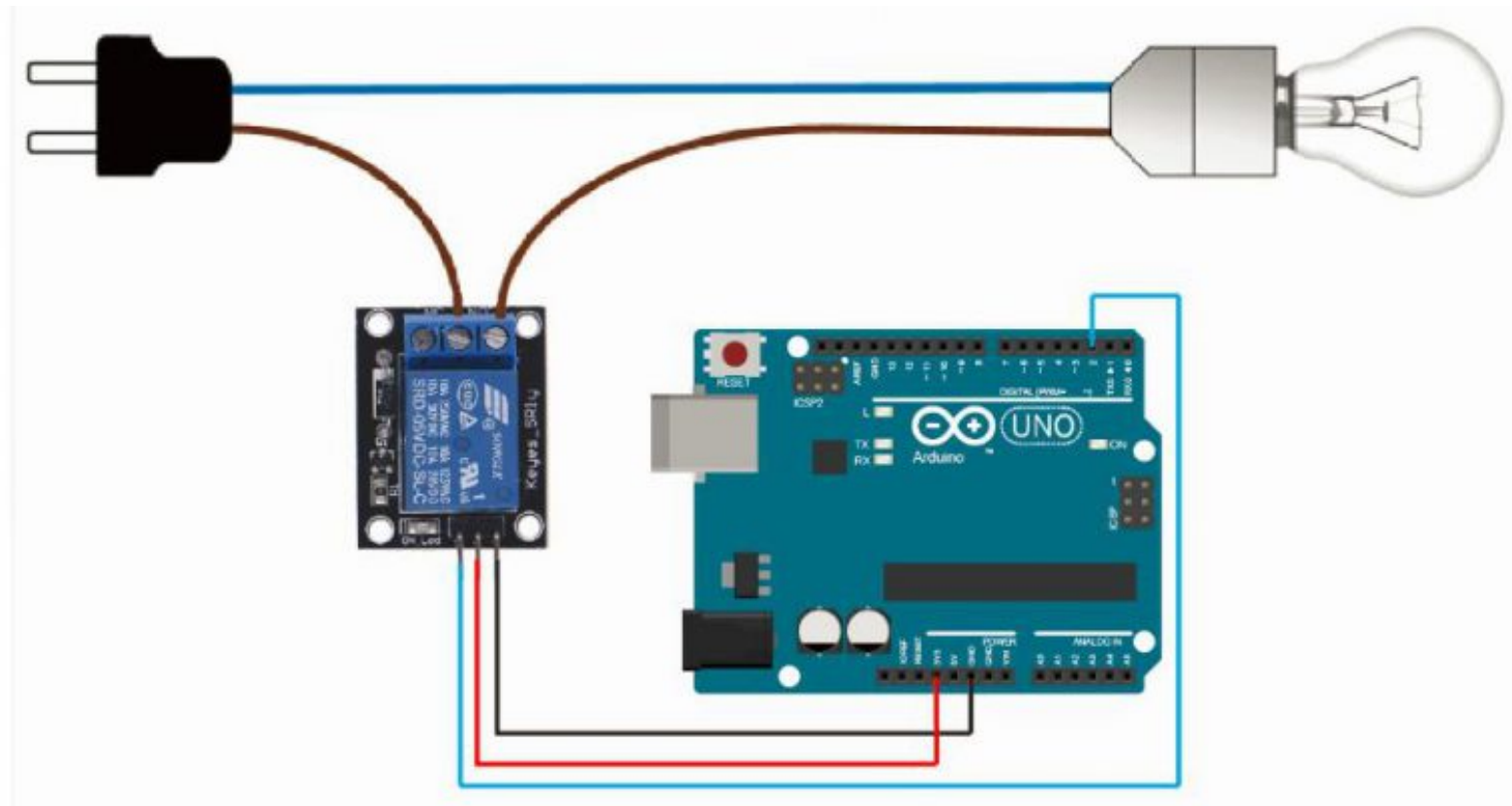

# MOSFET VS RELAY

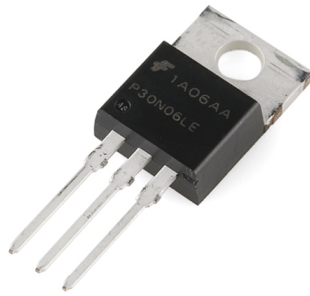

ANALOG AND DIGITAL  
ONLY DC POWER (400V)



DIGITAL  
DC (24V) AND AC (220V)

# ASSIGNMENT

Use NodeMCU to control a high power led and a motor.

Preparation: solder the wires to the DC Motor

Ex 1:

Control the High Power led with the MOSFET N-channel. Fade the light of the led using “analogWrite” command and “for” loop. Use the same circuit and code to control the motor.

Ex 2:

Control the dc motor using the relay. Using digital write command. Use the same circuit and code to control the High Power Led.

Extra:

Use one of the circuit of the previous exercise and send to your thing speak account the information of when the output device is on/off.

Document ex1, ex2 (and extra):

Document the process in your blog:

- schematic of the circuit
- code (readable)
- video

## LICENCE

EXCEPT WHERE OTHERWISE NOTED, THIS WORK IS LICENSED UNDER:

[HTTPS://CREATIVECOMMONS.ORG/LICENSES/BY/4.0/](https://creativecommons.org/licenses/by/4.0/)

