ELECTRONICS 1
ELECTRONICS FOR INTERACTIVE MEDIA DESIGN
LES 2

#### VOLTAGE - RESISTOR - CURRENT

A resistor is one of the most fundamental components in electronics. Its purpose is to <a href="impede">impede a flow of current</a> and <a href="impose a voltage reduction">impose a voltage reduction</a>.


Two wires or conductors attached at opposite ends or sides of a relatively poor electrical conductor.

The resistance of resistor is measured in ohms, universally represented by the Greek omega symbol,  $\Omega$ .

Ω	kΩ	MΩ
Ohms	Kilohms	Megohms
1	0.001	0.000001
10	0.01	0.00001
100	0.1	0.0001
1,000	1	0.001
10,000	10	0.01
100,000	100	0.1
1,000,000	1,000	1
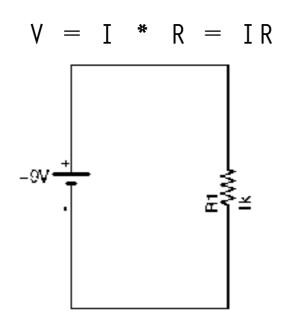
#### OHM'S LAW

Ohm's Law defines the relation between voltage, current and resistor



You know the Voltage and the Resistor => => calculate the current you consume: I = V / R

You know the Voltage and the Current => => calculate the resistor you will use: R = V / I

#### ELECTRIC POWER

In physics: power is defined as the rate at which <u>energy is transferred</u> <u>(or transformed)</u>. Unit of measure WATT (W).

<u>ENERGY</u> is basically the ability of something to move something else. Forms of energy: mechanical, electrical, chemical, electromagnetic, thermal, and many others.

TRANSFORMATION: energy can never be created or destroyed, only transferred to another form. A lot of what we're doing in electronics is converting different forms of energy to and from electric energy.

Energy type converted	Converted by
Mechanical	Electric Motor
Electromagnetic	LED
Heat	Resistor
Chemical	Battery
Wind	Windmill

Electric power is measured by combining both <u>how much electric energy</u> is transferred, and <u>how fast that transfer</u> happens.


#### ELECTRIC POWER FOR RESISTORS

how much electric energy is transferred: Voltage
how fast that transfer happens: Current

Unit of measure: Watt (W)

P = V \* I = VI

#### ELECTRIC POWER FOR RESISTORS

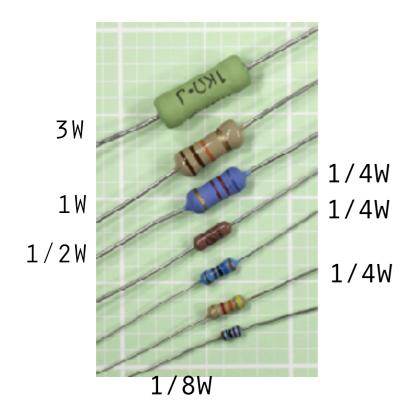

$$P = VI$$
 or 
$$P = RI *I = RI^{2}$$
 or 
$$P = V * V/R = V^{2}/R$$
 The most common power rating is  $1/4W = 0.25W$ 


In case of resistors electric energy is converted to heat.







## POWER EXAMPLES

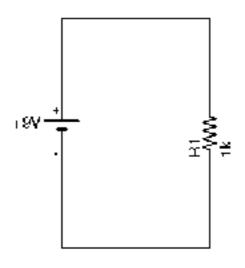

V = 9 V R = 1K OHMI = 0.009 A


V = 9 V R = 10 OHMI = 0.9 A

P = 0.081W

P = 810W
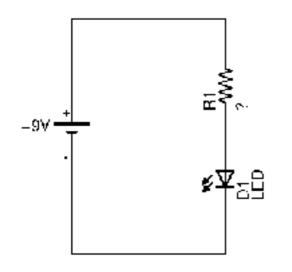
#### CIRCUIT LED

HOW TO USE OHM'S LAW IN THE DESIGNING OF MY CIRCUIT?



Luminous Intensity:




32 mcd

#### Specifications from Datasheet:

- wavelength of emitted light
- luminous intensity
- maximum forward voltage and current
- maximum reverse voltage and current,
- working values for voltage and current

#### Productgegevens Viewing Angle: LED Colour: 68° Red **LED Mounting:** Through Hcle Lens Shape: Round Bulb Size: T-1 3/4 (5mm) Packaging: Each Forward Current If: Product Range: 25mA Forward Voltage: 1.77 **Automotive Qualification** Standard: Wavelength Typ: 660nm MSL:
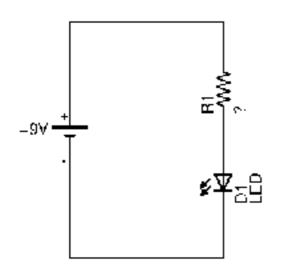
# CIRCUIT LED HOW TO CALCULATE THE RESISTOR





#### Specifications:

- working values for voltage and currentVf = 1.7V

  - If = 25mA

$$R = (V_{CC} - V_F) / I$$


$$R = (V_{CC} - V_F) / I$$
  $R = (9 - 1.7)/0.025 = 292 0 HM ~ 300 0 HM$ 

#### CIRCUIT LED

Typical forward voltages for various colours are, typical current 20mA:

- Infrared LED: 1.6V to 2V
- Red LED: 1.6V to 2.1V
- Orange LED: 1.9V to 2.1V
- Amber LED: 2V to 2.1V
- Yellow LED: 2V to 2.4V
- Green LED: 2.4V to 3.4V
- Blue LED: 3.2V to 3.4V
- Ultraviolet LED: 3.3V to 3.7V
- White LED: 3.2V to 3.6V

# CIRCUIT LED ANALISYS

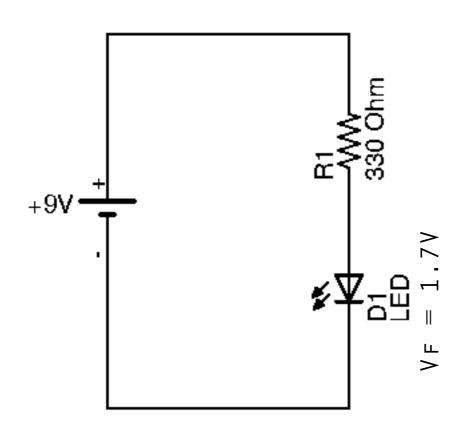

$$I = (Vcc - Vf) / R = 22mA$$

Power of the resistor:  

$$P_R = (Vcc - Vf)*I = 160mW$$

Power of the LED:  

$$P_{LED} = Vf * I = 37mW$$

#### ARDUINO

"Physical Computing is about prototyping with electronics, turning sensors, actuators and microcontrollers into materials for designers and artists."

"It involves the design of interactive objects that can communicate with humans using sensors and actuators controlled by a behaviour implemented as software running inside a microcontroller."

Massimo Banzi, Tinker.it & Arduino Co-Founder


HARDWARE



SOFTWARE




COMMUNITY

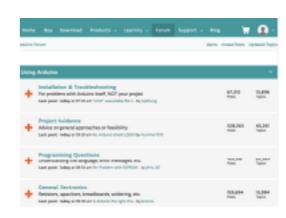


#### ARDUINO - POWER PINS

#### POWER PINS

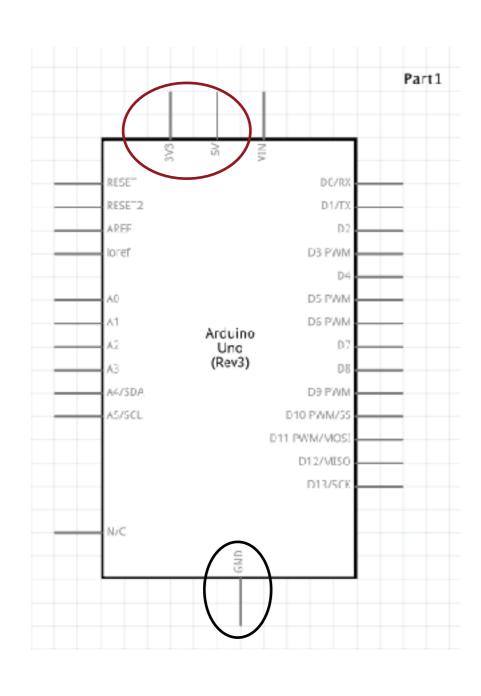

5V / 3.3V: Power


GND: GROUND PIN

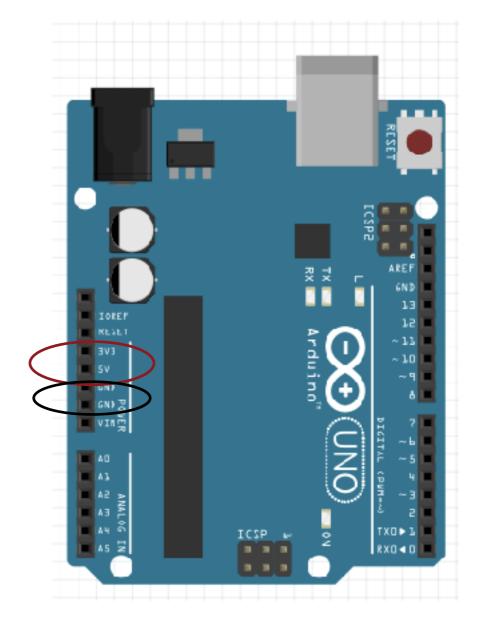

## BREADBOARD

WIRE - WRAP




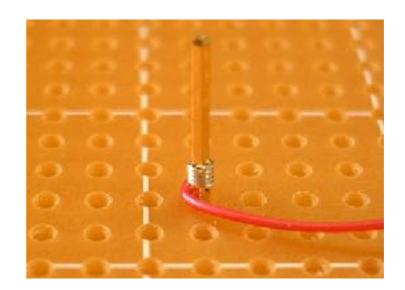


BREADBOARD






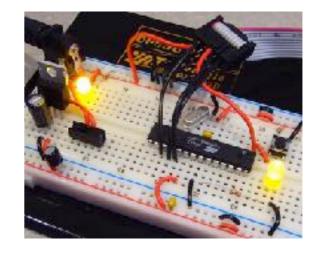


# ARDUINO

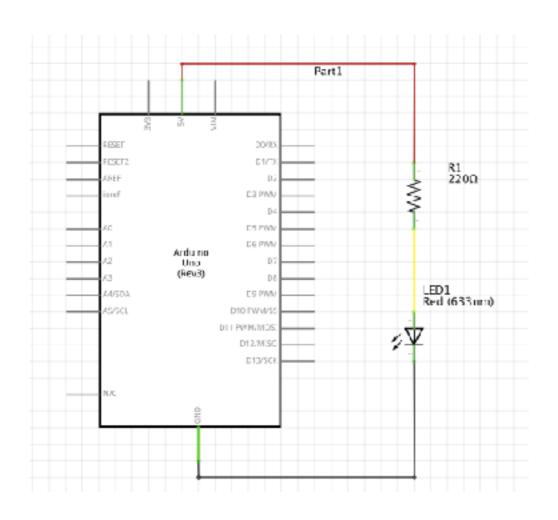


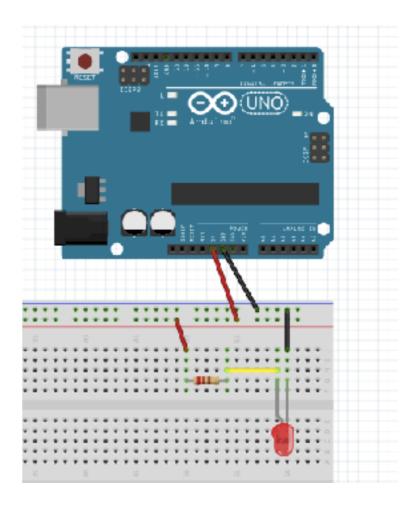


#### BREADBOARD

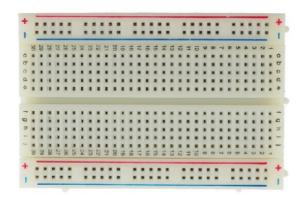


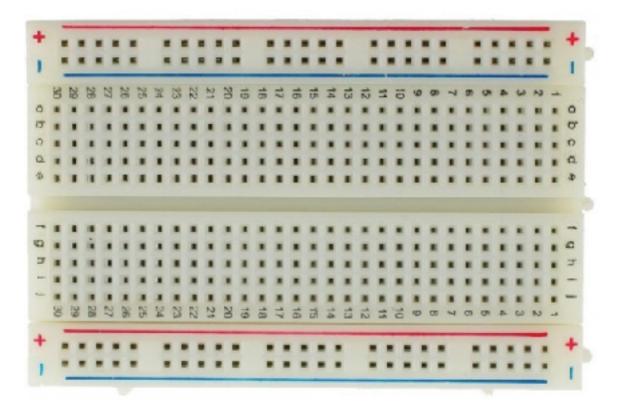IT IS A PHYSICAL SUPPORT FOR MAKING TEMPORARY CIRCUITS AND PROTOTYPING, AND THEY REQUIRE ABSOLUTELY NO SOLDERING.




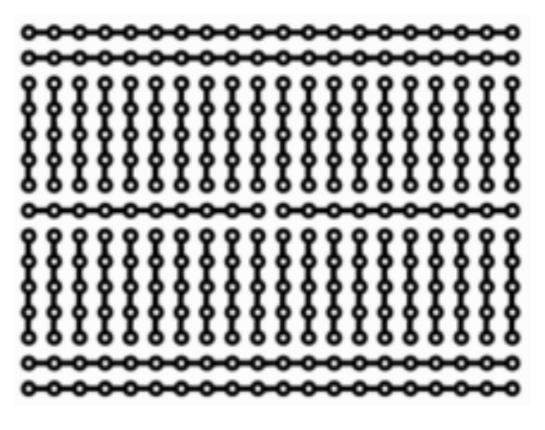


#### BREADBOARD - BEST PRACTICE

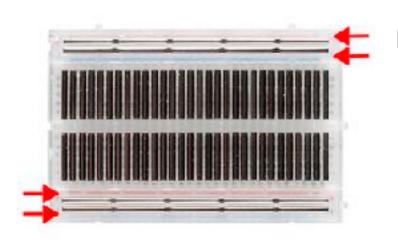



POWER RAILS

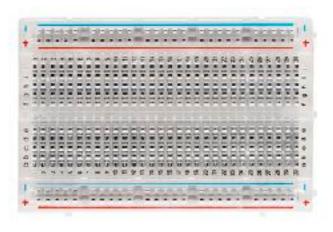

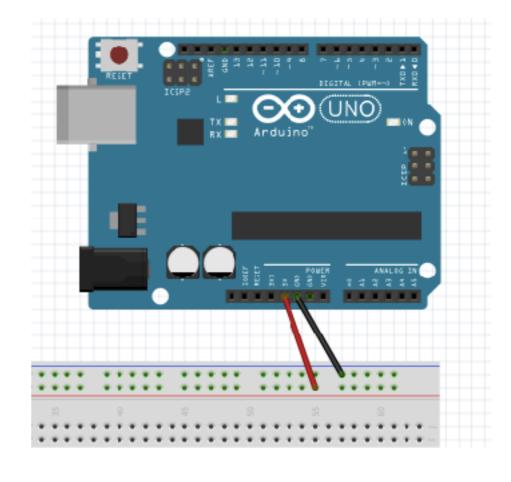


#### ARDUINO

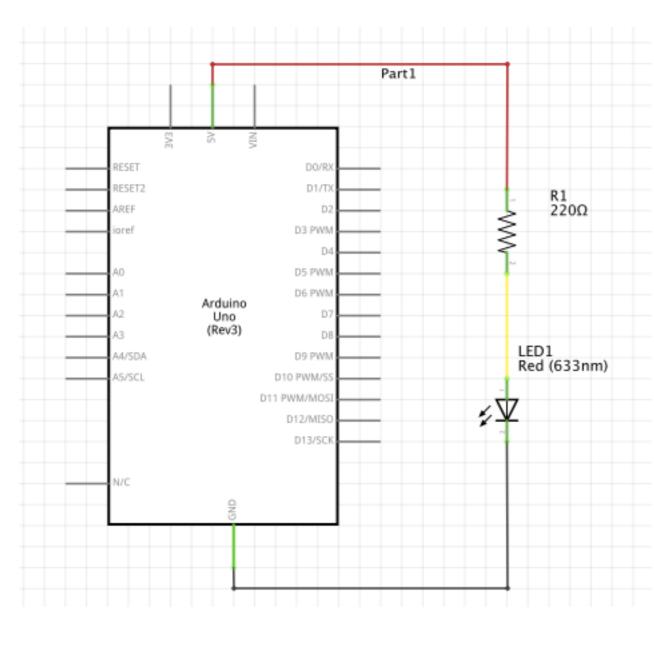

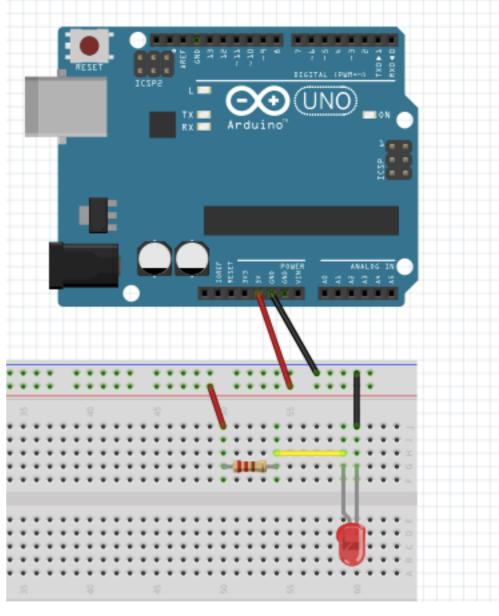


#### ARDUINO

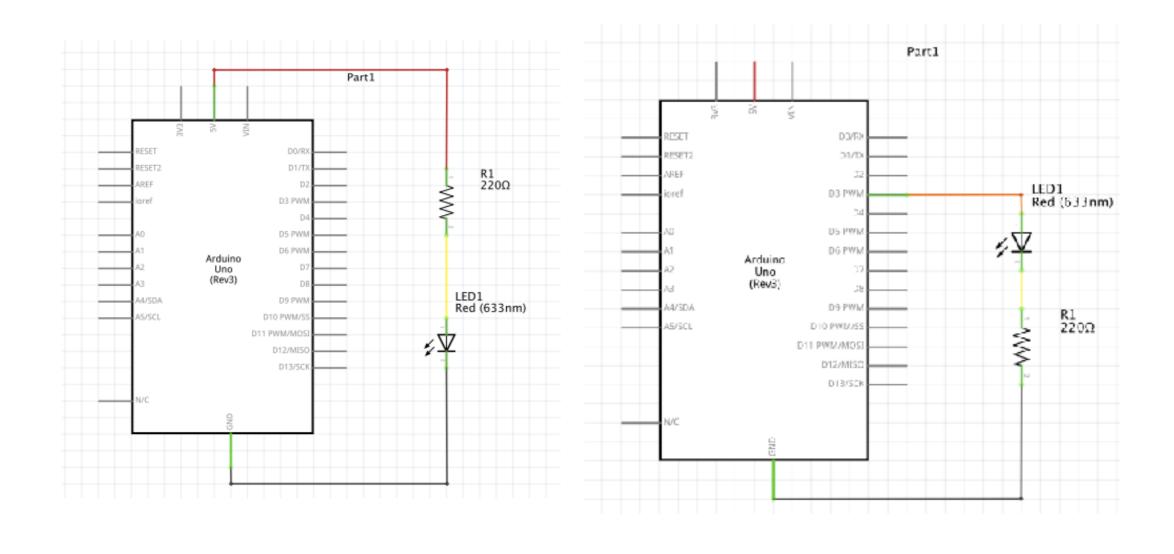


#### INPUT/OUTPUT PIN

PIN IO (INPUT/OUTPUT) Part1 Digital Pins RESE<sup>2</sup> ionef D3 P/VN Digital Pwm Pins **Analog Pins** D5 PWN DS PWN Arduino Uno (Rev3) 10 PWM/5 PWM/MOS

## CONTROL A LED WITH ARDUINO

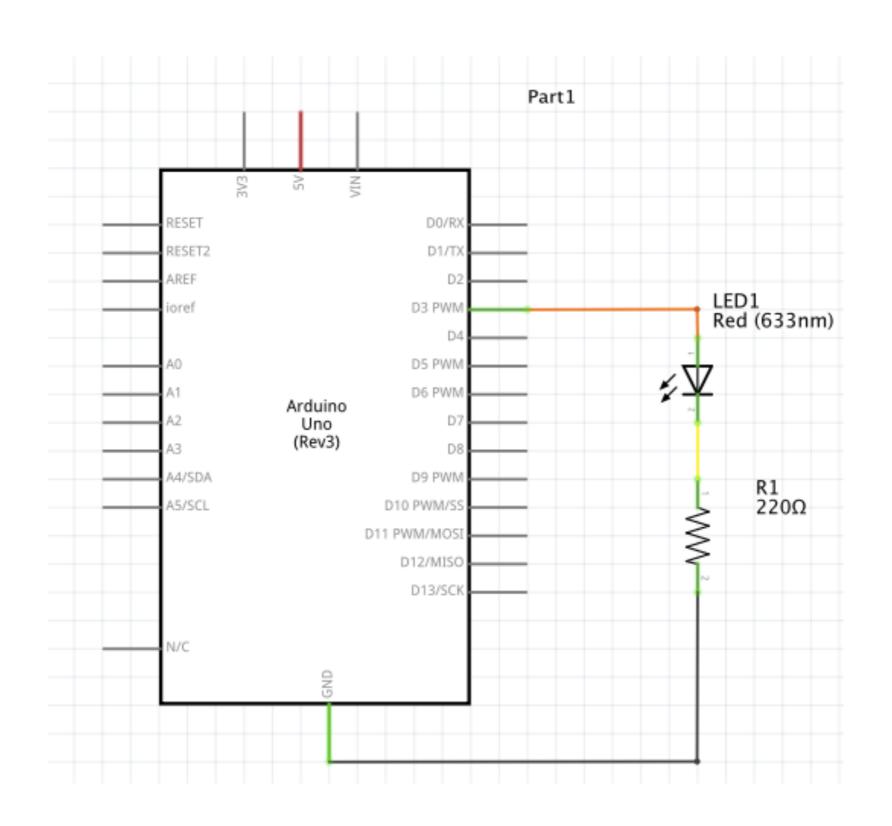
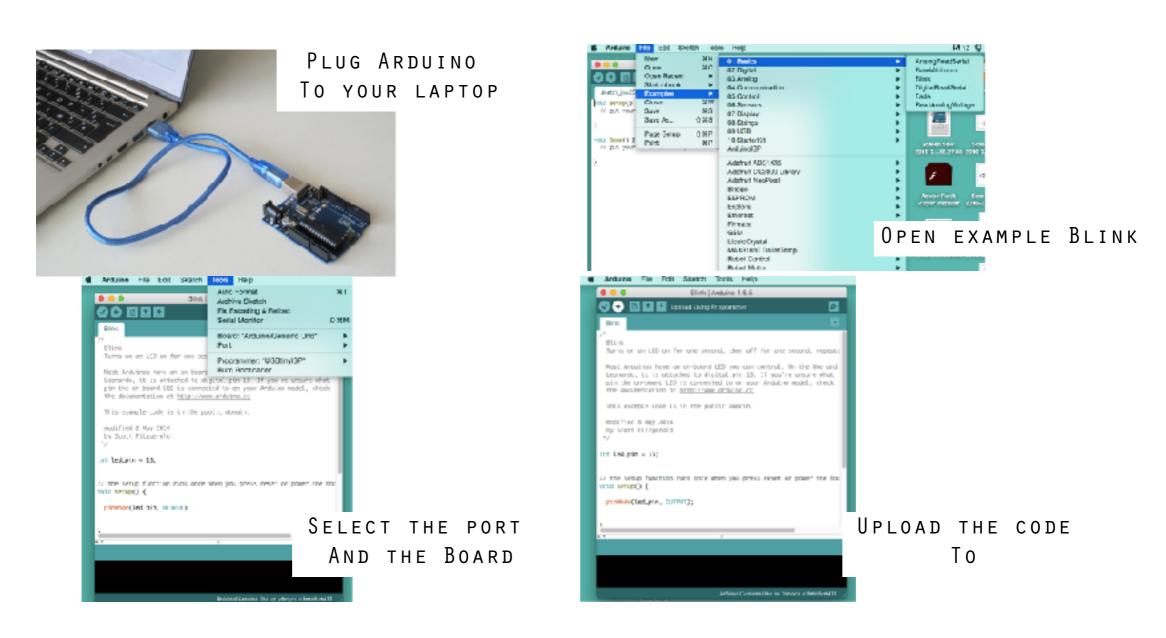
#### BUT...CHECK IF THE ENVIRONMENT WORKS



IF IT WORKS, THE LED EMBEDDED ON THE BOARD BLINKS

#### SKETCH

GLOBAL VARIABLES DECLARE THE VARIABLES INITIALISE SETUP() RUNS ONCE, AT THE BEGINNING DEFINE THE PINS RUNNING L00P() RUN REPEATEDLY, AFTER SETUP

Done Saving.

The sketch name had to be modified. Sketch names can only consist of ASCII characters and numbers (but cannot start with a number).

They should also be less than 64 characters long.


\_01\_blink | Arduino 1.6.9

SETUP()
DEFINE THE FUNCTION OF THE
PIN
PINMODE(PIN, FUNCTION);

THE PIN IS 'LED\_PIN
THE FUNCTION IS OUTPUT



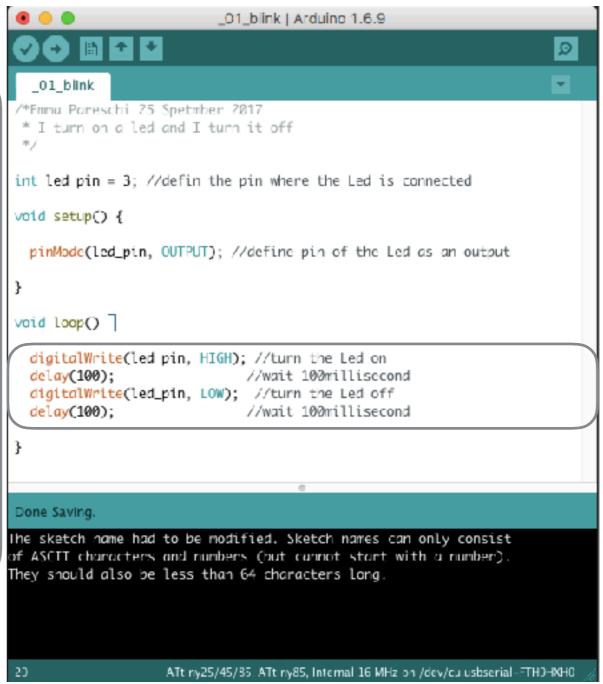
# LOOP() THE LIST OF COMMANDS THAT ARDUINO RUNS REPEATEDLY. DIGITALWRITE(PIN, LEVEL); WE CONTROL THE VOLTAGE ON THE PIN HIGH: HIGH VOLTAGE (5V) LOW: LOW VOLTAGE (GROUND) DELAY(TIME); WE ADD A DELAY IN MILLISECOND







#### CONNECT, COMPILE AND UPLOAD

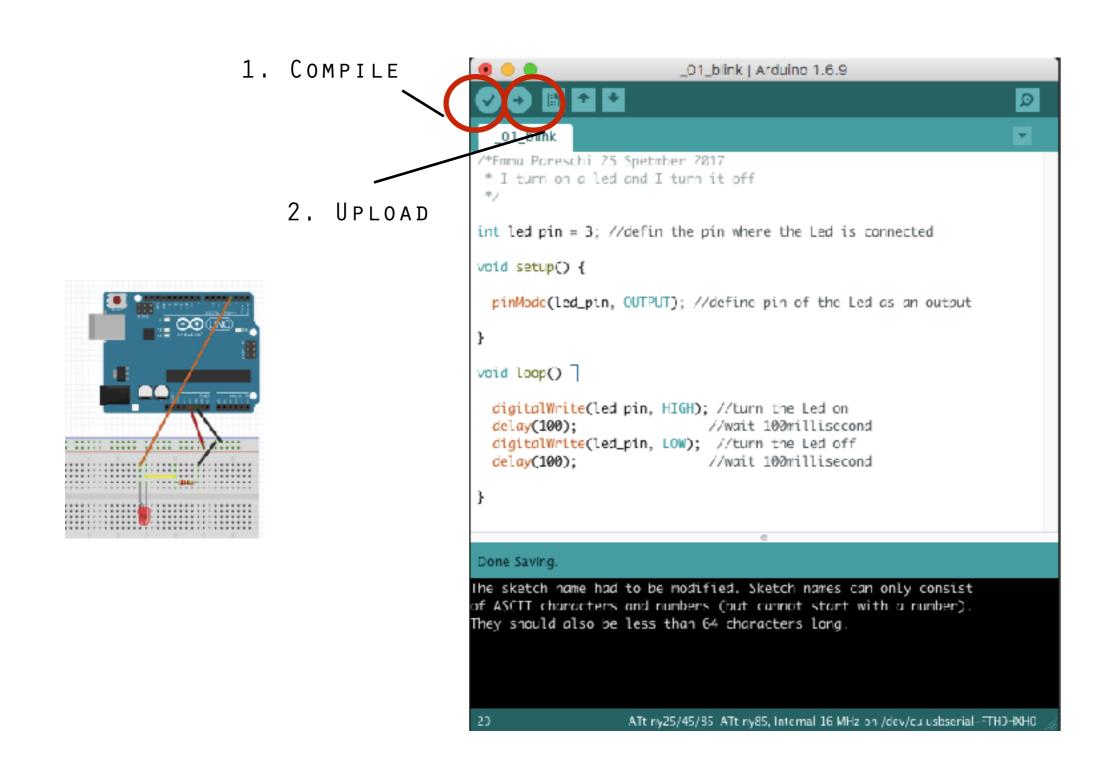

#### CONTROL THE INTENSITY OF THE LED

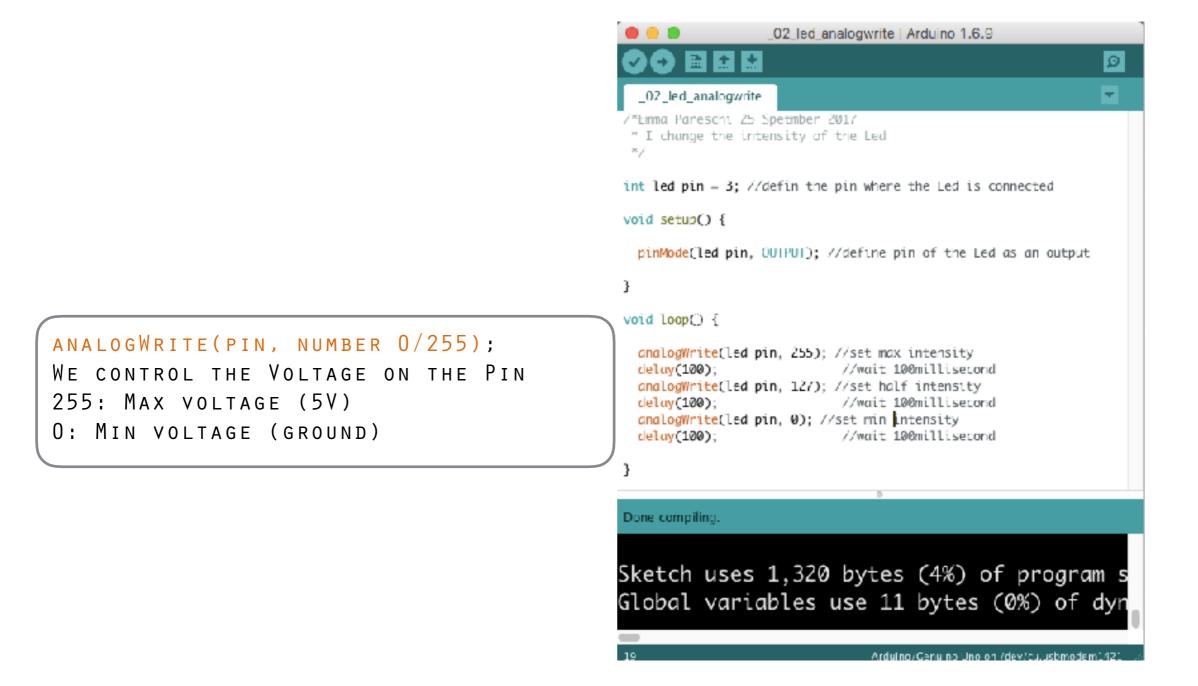



#### PWM PINS

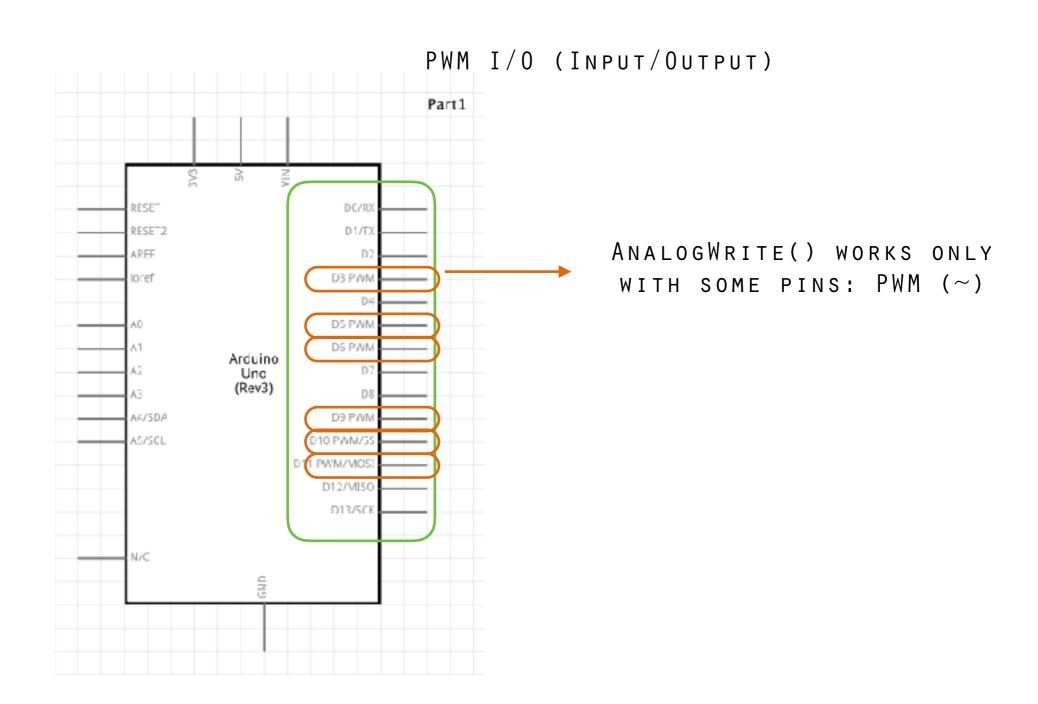

#### PWM


#### Pulse-width modulation

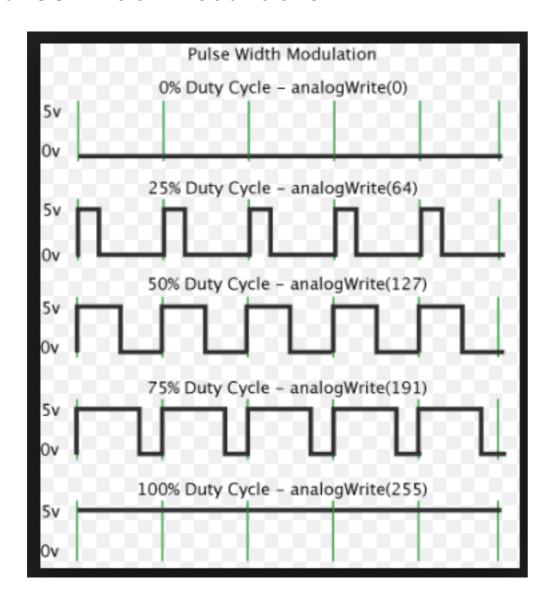

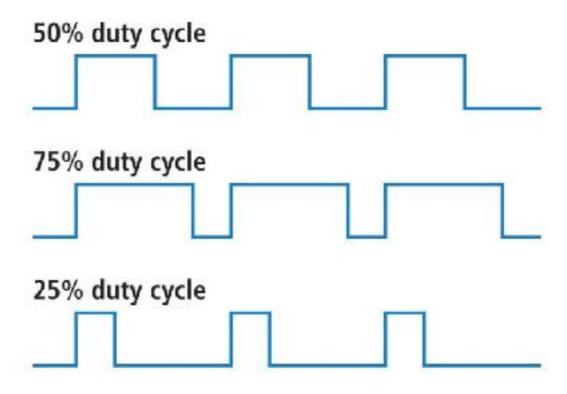


#### PWM


#### Pulse-width modulation

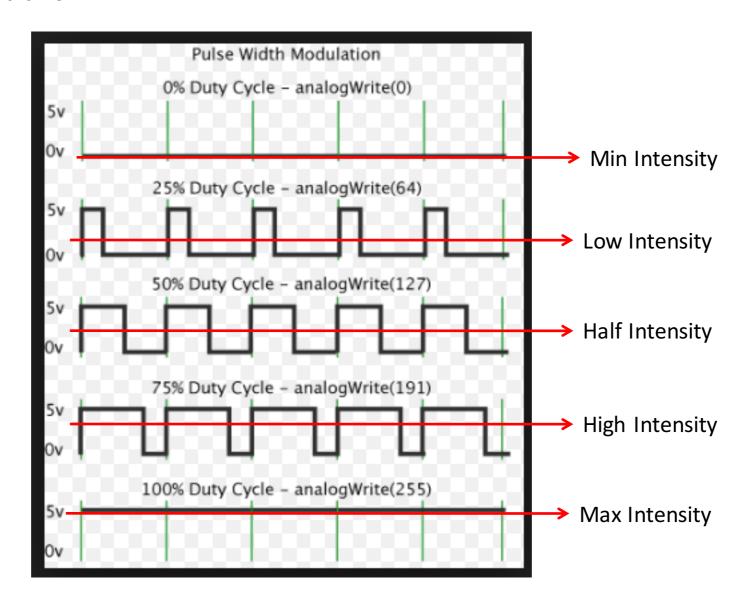


#### HOW TO READ A SENSOR (DIGITAL)

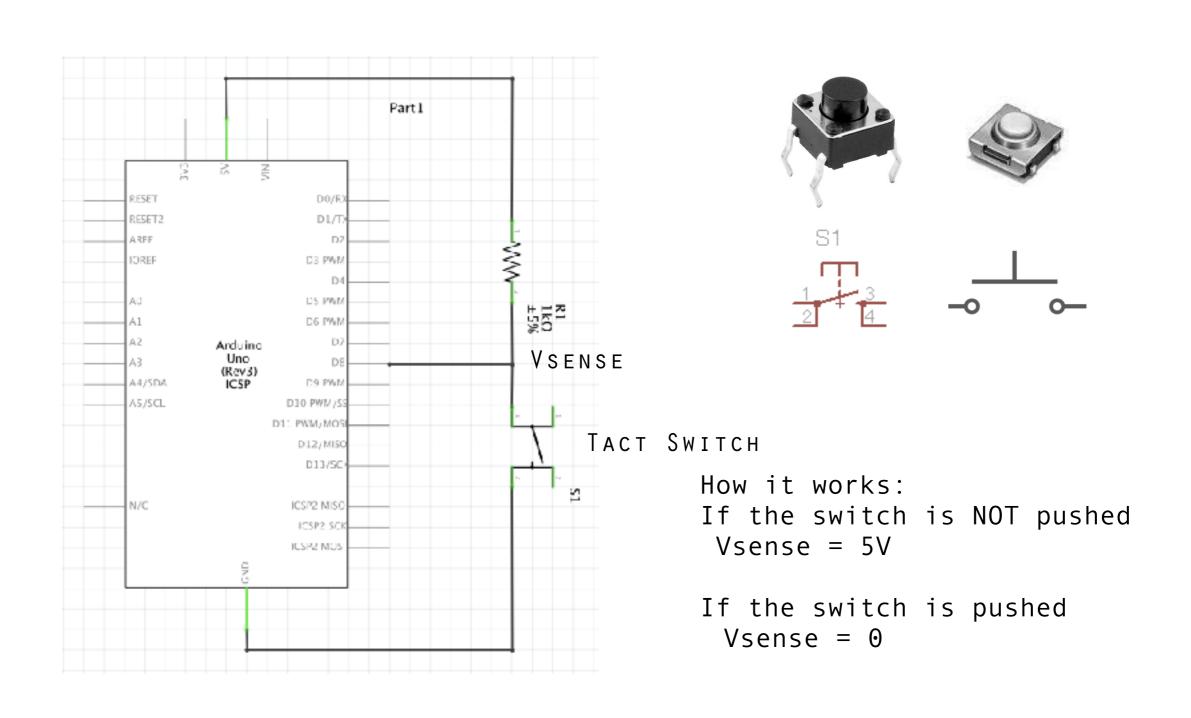

#### HOW TO READ A SENSOR (DIGITAL)

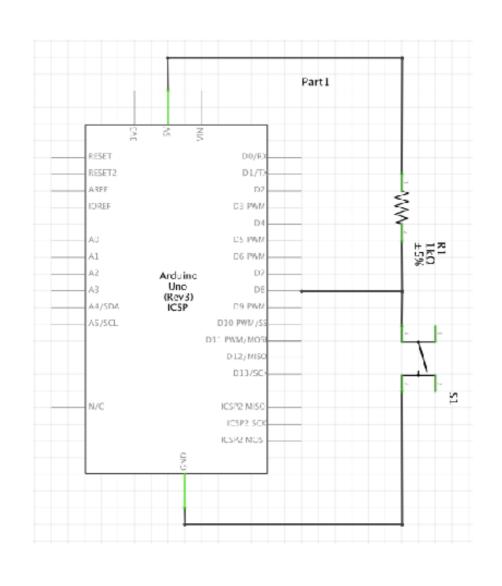

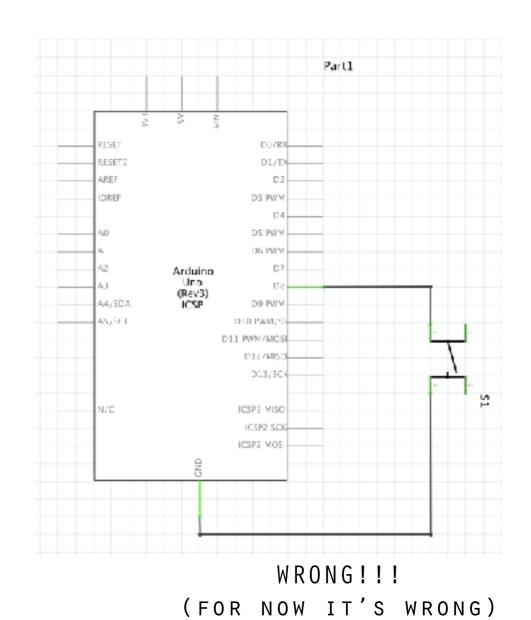

#### SKETCH - READ A SENSOR (DIGITAL)

```
_03_sw | Arduino 1.6.9
  03 sw §
∕* Emma Pareschi
 * Septmber 2017
 * I read the value of a tact switch (or pushbutton)
// constants won't change. They're used here to
                                                               sw_pin: to define the switch pin
// set pin numbers:
const int sw_pin = 8; // the number of the pushbutton pin
// variables will change:
                                                               sw state: to save the data
int sw_state = 0; // variable for reading the pushbutton status
void setup() {
 // initialize the pushbutton pin as an input:
                                                               pinMode INPUT
 pinMode(sw_pin, INPUI);
}
void loop() {
 // read the state of the pushbutton value:
                                                               Function to read the value of the pin
 sw state = digitalRead(sw pin);
 delay(100);
```

# SKETCH - READ A SENSOR (DIGITAL) AND TO PRINT THE VALUES

```
03 sw | Arduino 1.6.9
/* Emma Pareschi

    Septmber 2017


    I read and print on the computer

    the value of a tact switch (or pushbutton)

// constants won't change. They're used here to
// set pin numbers:
const int sw pin = 8; // the number of the pushbutton pin
// variables will change:
int sw_state = 0;
                      // variable for reading the pushbutton status
void setup() {
 // initialize the pushbutton pin as an input:
 pinMode(sw_pin, INPUT);
 //open the serial communication with the laptop
                                                                                To open communication
  Scrial.begin(9700);
void loop() {
 // read the state of the pushbutton value:
 sw_state = digitalRead(sw_pin);
 //print on the serial Monitor
| Serial.print("The value of the switch is: ");
                                                                                To print on serial monitor
 Serial.println(sw_state);
 //add a delay
 dclay(100);
```

# TURN ON/OFF THE LED BASED ON THE SWITCH

..NEXT TIME..

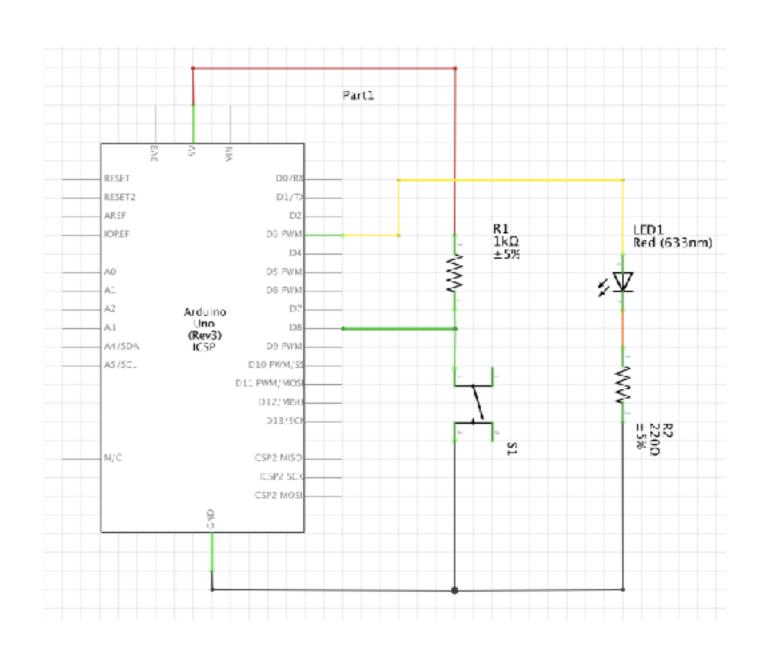

#### SKETCH - LED AND SWITCH

..NEXT TIME..


```
// constants won't change. They're used here to
// set pin numbers:
const int buttonPin = 2;
                            // the number of the pushbutton pin
                            // the number of the LED pin
const int ledPin = 13;
// variables will change:
int buttonState = 0;
                            // variable for reading the pushbutton sta
void setup() {
 // initialize the LED pin as an output:
  pinMode(ledPin, OUTPUT);
  // initialize the pushbutton pin as an input:
  pinMode(buttonPin, INPUT);
}
void loop() {
 // read the state of the pushbutton value:
  buttonState = digitalRead(buttonPin);
 // check if the pushbutton is pressed.
  // if it is, the buttonState is HIGH:
  if (buttonState == HIGH) {
   // turn LED on:
    digitalWrite(ledPin, HIGH);
  } else {
    // turn LED off:
    digitalWrite(ledPin, LOW);
```

```
Control Structure 'if..else':

if (this condition happens)
{
    // action A
}
else
{
    // action B
}
```

#### HOW TO READ A SENSOR (ANALOG)

..NEXT TIME..

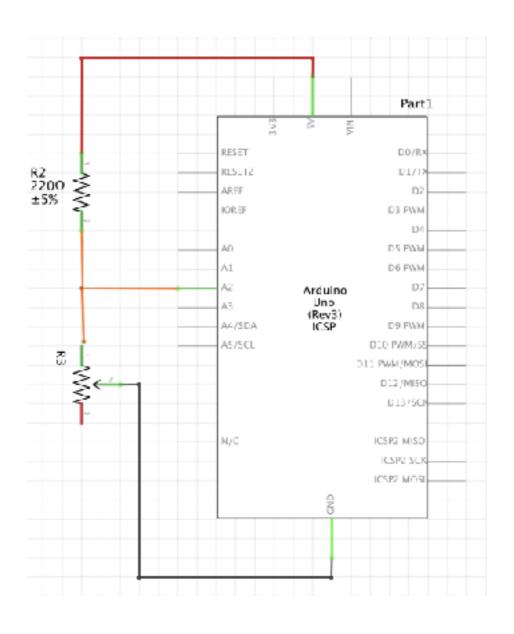

#### ASSIGNMENTS

- 1) Design and program a circuit with the following specifications:
  - at least two LEDs
  - use the functions digitalWrite and analogWrite
- 2) Design and program a circuit with the following specifications:
  - at least one tact switch
  - use the functions digitalRead, Serial.print and Serial.println

More information about Serial.print: <a href="https://www.arduino.cc/en/Serial/Print">https://www.arduino.cc/en/Serial/Print</a> Serial.println: <a href="https://www.arduino.cc/en/Serial/Println">https://www.arduino.cc/en/Serial/Println</a>

- 3) Document the two projects in your blog with two posts, the documentation includes:
  - a short description of the functionality of the circuit
  - schematic of the circuit
  - sketch (arduino code)
  - if it works: upload a video of the circuit that works
  - if it doesn't work: explain what you did to debug hardware and software

Note: if you take inspiration or you reproduce a circuit/code done by someone else, you have to acknowledge the source in your post.

#### ONLINE CALCULATORS

HTTP://WWW.OHMSLAWCALCULATOR.COM/OHMS-LAW-CALCULATOR

HTTP://WWW.OHMSLAWCALCULATOR.COM/LED-RESISTOR-CALCULATOR

HTTP://WWW.OHMSLAWCALCULATOR.COM/VOLTAGE-DIVIDER-CALCULATOR

#### Sources and Licence

Ohm's Law:

https://learn.sparkfun.com/tutorials/voltage-current-resistance-and-ohms-law

Electric Power:

https://learn.sparkfun.com/tutorials/electric-power

Resistors (pg.75)

Encyclopedia of Electronic Components Volume 1, 1st Edition, Charles Platt

Leds (pg. 205)

Encyclopedia of Electronic Components Volume 2, 1st Edition, Charles Platt.

Arduino commands:

https://www.arduino.cc/en/Reference/HomePage

#### LICENCE

EXCEPT WHERE OTHERWISE NOTED, THIS WORK IS LICENSED UNDER: <a href="https://creativecommons.org/licenses/by/4.0/">https://creativecommons.org/licenses/by/4.0/</a>

